

VLSI Lab Report

COURSE CODE: EC362

Cadence Virtuoso Report



Submitted by:

Name: Aditya Krishna Jaiswal
Roll Number: 2201011

Department of Electronics and Communication Engineering
Indian Institute of Information Technology Guwahati

Date of submission: April 13, 2025

Index

1. Verification of Input and Output Characteristics of an NMOS Transistor
2. Verification of Input and Output Characteristics of a PMOS Transistor
3. Analysis of DC, AC, and Transient Response of a CS Amplifier
4. Analysis of DC and Transient Response of a CMOS Inverter
5. Analysis of DC Voltage Transfer Characteristics and Truth Table Verification of NAND and NOR Gates
6. Symbol Formation and Truth Table Verification for NAND, NOR, D Flip-Flop, and NOT Gates
7. Implementation and Analysis of a Current Mirror Circuit

Experiment-1: Verification of Input and Output Characteristics of an NMOS Transistor

Introduction

The aim of this experiment is to verify both the input and output characteristics of an NMOS transistor and to plot the corresponding graphs. The NMOS (N-channel Metal-Oxide-Semiconductor) transistor is a key component in modern electronics, extensively utilized in amplification and switching applications. Understanding its electrical characteristics is essential for designing and analyzing electronic circuits. This experiment involves measuring the drain current under varying voltage conditions to validate theoretical predictions and assess the transistor's operational behavior.

Theory

The NMOS transistor's behavior is governed by the relationship between its drain current (I_D), gate-to-source voltage (V_{GS}), and drain-to-source voltage (V_{DS}). These relationships define two primary characteristics:

Input Characteristics

The input characteristics describe the variation of drain current (I_D) with gate-to-source voltage (V_{GS}) while maintaining a constant drain-to-source voltage (V_{DS}). When V_{GS} exceeds the threshold voltage (V_t), the transistor enters the saturation region, and I_D increases quadratically according to the MOSFET equation:

$$I_D = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

where: - μ_n : electron mobility, - C_{ox} : oxide capacitance per unit area, - W : channel width, - L : channel length, - V_t : threshold voltage.

This quadratic relationship highlights the transistor's sensitivity to V_{GS} in the saturation region.

Output Characteristics

The output characteristics depict the variation of I_D with V_{DS} for a fixed V_{GS} . Two distinct regions are observed: 1. Linear Region: When $V_{DS} < (V_{GS} - V_t)$, I_D increases linearly with V_{DS} , described by:

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2 \right]$$

2. Saturation Region: When $V_{DS} \geq (V_{GS} - V_t)$, I_D becomes nearly constant, primarily controlled by V_{GS} , as shown in the saturation equation above.

These characteristics enable the NMOS transistor to function effectively as an amplifier or switch, depending on the operating region.

Methodology

The experimental setup involved an NMOS transistor configured with appropriate resistors and voltage sources to measure its characteristics: - Input Characteristics: V_{DS} was held constant, and V_{GS} was varied incrementally. The resulting I_D was recorded for each V_{GS} value. - Output Characteristics: V_{GS} was fixed at several discrete values, and V_{DS} was swept across a range. The corresponding I_D was measured.

The circuit configuration is illustrated in Figure 29.

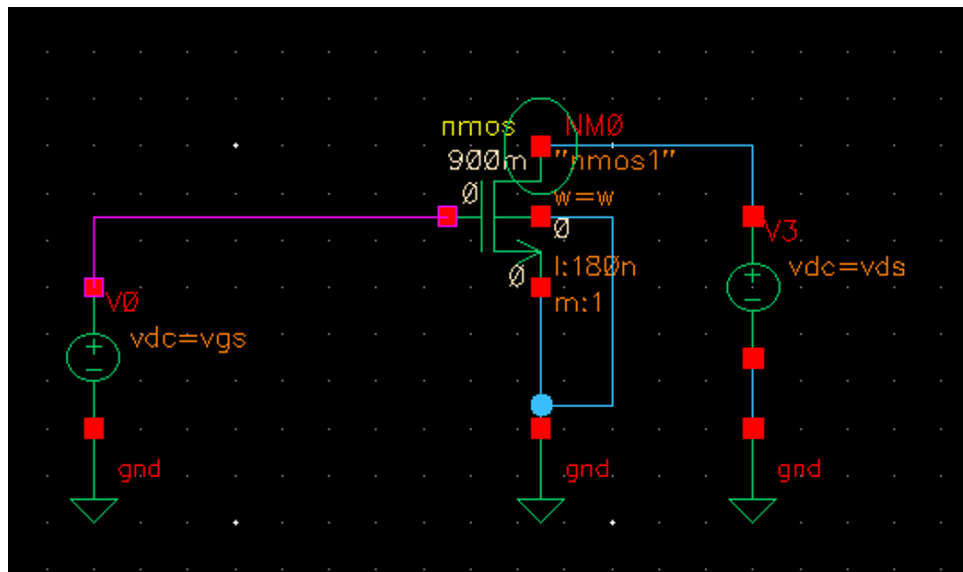


Figure 1: Circuit Diagram for NMOS Characteristics Measurement

Results

The experimental data were plotted to visualize the NMOS transistor's behavior. The results are presented in the following figures: - Figure 7: Input characteristic curve showing I_D versus V_{GS} . - Figure 8: Parametric input characteristic, likely illustrating I_D versus V_{GS} under varying conditions (e.g., different V_{DS} values). - Figure 9: Output characteristic curves displaying I_D versus V_{DS} for multiple fixed V_{GS} values. - Figure 10: Parametric output characteristic, possibly showing additional parameter variations.

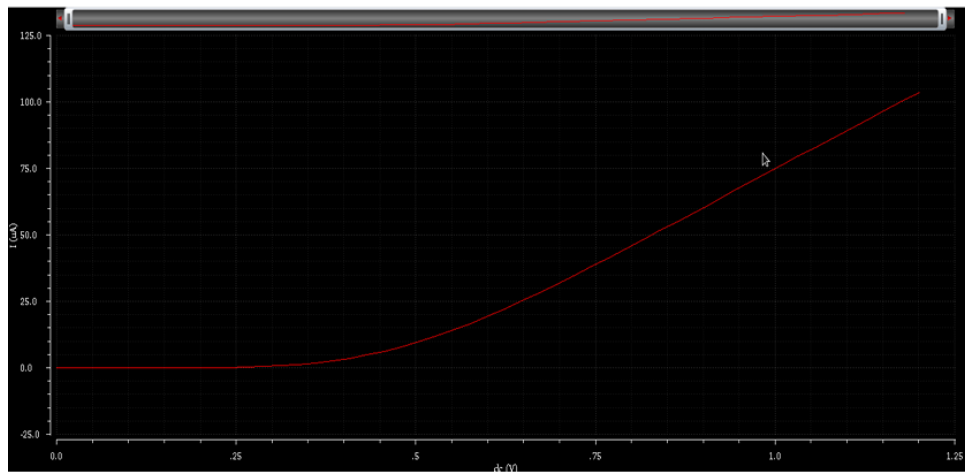


Figure 2: Input Characteristic: I_D vs. V_{GS} for NMOS Transistor

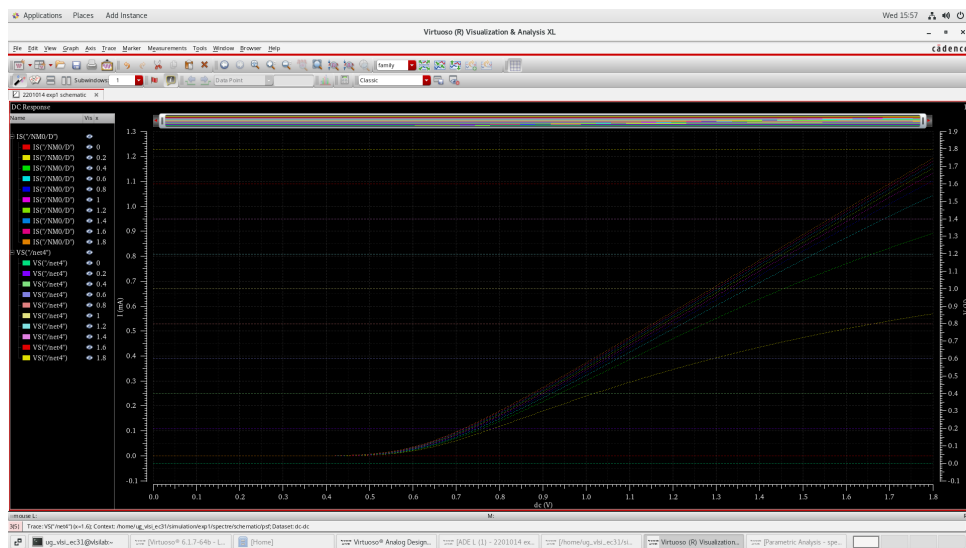


Figure 3: Parametric Input Characteristic: I_D vs. V_{GS} for NMOS Transistor

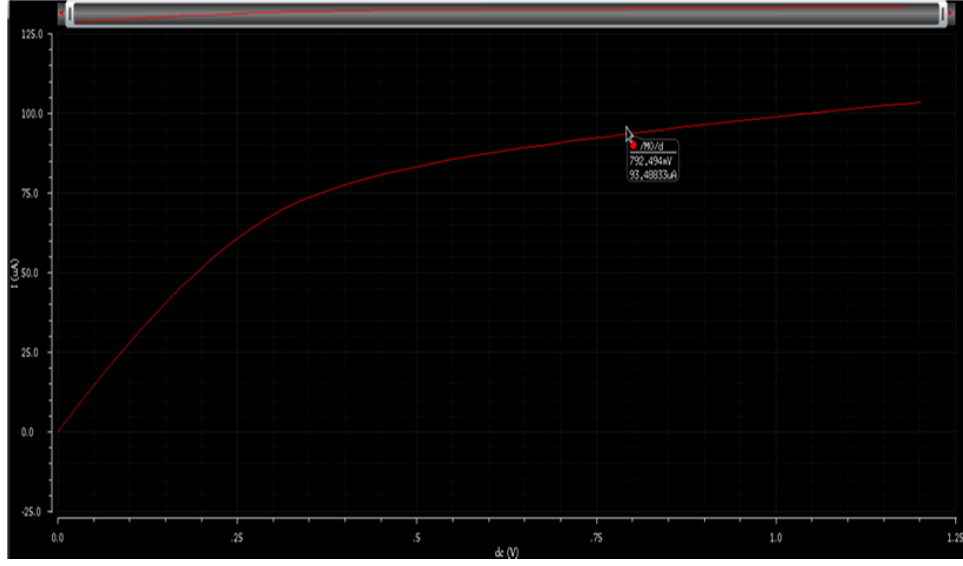


Figure 4: Output Characteristic: I_D vs. V_{DS} for NMOS Transistor

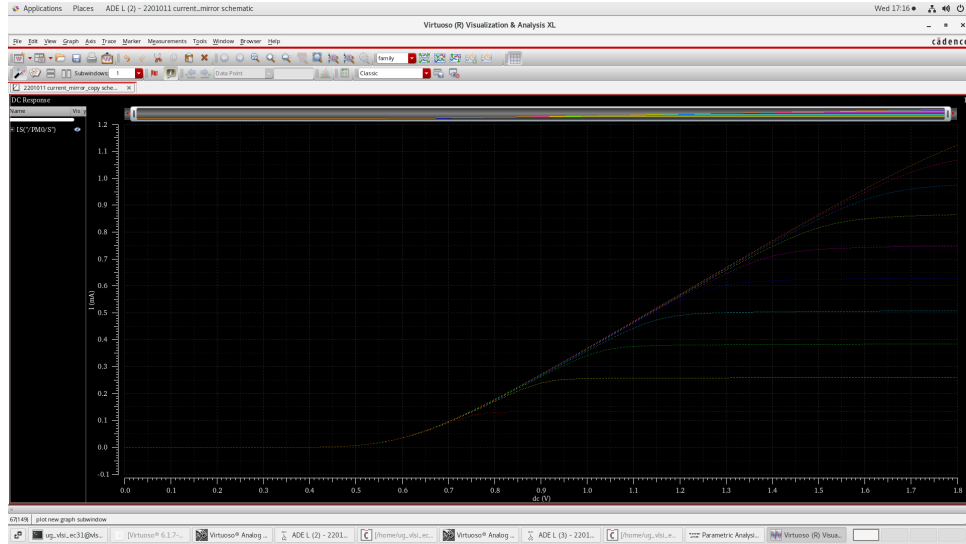


Figure 5: Parametric Output Characteristic: I_D vs. V_{DS} for NMOS Transistor

Discussion

The input characteristic curve (Figure 7) exhibits a quadratic increase in I_D with V_{GS} beyond the threshold voltage, consistent with the theoretical saturation region behavior. This confirms the NMOS transistor's operation as predicted by the MOSFET equation.

The output characteristic curves (Figure 9) illustrate a clear transition from the linear region, where I_D rises with V_{DS} , to the saturation region, where I_D stabilizes. This behavior aligns with the expected performance for different V_{GS} values, underlining the transistor's utility in amplification applications.

The parametric plots (Figures 8 and 10) provide deeper insights, potentially showing how additional variables (e.g., temperature or device parameters) affect the characteristics. These results reinforce the theoretical framework and validate the experimental methodology.

Conclusion

This experiment successfully verified the input and output characteristics of an NMOS transistor. The input characteristics demonstrated a quadratic rise in drain current (I_D) with increasing gate-to-source voltage (V_{GS}) beyond the threshold voltage, confirming saturation region behavior. The output characteristics revealed distinct linear and saturation regions as drain-to-source voltage (V_{DS}) varied, consistent with theoretical expectations for fixed V_{GS} values. These findings validate the MOSFET's operational principles and affirm its applicability in amplification and switching circuits.

Experiment-2: Verification of Input and Output Characteristics of a PMOS Transistor

Introduction

The aim of this experiment is to verify both the input and output characteristics of a PMOS transistor and to plot the corresponding graphs. The PMOS (P-channel Metal-Oxide-Semiconductor) transistor is a key component in modern electronics, widely used in amplification and switching applications. Understanding its electrical characteristics is essential for designing and analyzing electronic circuits. This experiment involves measuring the drain current under varying voltage conditions to validate theoretical predictions and assess the transistor's operational behavior.

Theory

The PMOS transistor's behavior is governed by the relationship between its drain current (I_D), gate-to-source voltage (V_{GS}), and drain-to-source voltage (V_{DS}). These relationships define two primary characteristics:

Input Characteristics

The input characteristics describe the variation of drain current (I_D) with gate-to-source voltage (V_{GS}) while maintaining a constant drain-to-source voltage (V_{DS}). When V_{GS} becomes sufficiently negative (below the threshold voltage V_t , which is negative for PMOS), the transistor enters the saturation region, and I_D increases quadratically according to the MOSFET equation:

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_t|)^2$$

where: - μ_p : hole mobility, - C_{ox} : oxide capacitance per unit area, - W : channel width, - L : channel length, - V_t : threshold voltage (negative for PMOS), - $V_{SG} = -V_{GS}$ (source-to-gate voltage, positive when V_{GS} is negative).

This quadratic relationship highlights the transistor's sensitivity to V_{GS} in the saturation region, with current flowing when $V_{GS} < V_t$.

Output Characteristics

The output characteristics depict the variation of I_D with V_{DS} for a fixed V_{GS} . Two distinct regions are observed: 1. Linear Region: When $V_{SD} < (V_{SG} - |V_t|)$ (or $V_{DS} > (V_{GS} + |V_t|)$ due to PMOS polarity), I_D increases linearly with V_{DS} , described by:

$$I_D = \mu_p C_{ox} \frac{W}{L} \left[(V_{SG} - |V_t|) V_{SD} - \frac{1}{2} V_{SD}^2 \right]$$

where $V_{SD} = -V_{DS}$.

2. Saturation Region: When $V_{DS} \leq (V_{GS} + |V_t|)$, I_D becomes nearly constant, primarily controlled by V_{GS} , as shown in the saturation equation above.

These characteristics enable the PMOS transistor to function effectively as an amplifier or switch, depending on the operating region.

Methodology

The experimental setup involved a PMOS transistor configured with appropriate resistors and voltage sources to measure its characteristics: - Input Characteristics: V_{DS} was held constant, and V_{GS} was varied incrementally in the negative direction. The resulting I_D was recorded for each V_{GS} value. - Output Characteristics: V_{GS} was fixed at several discrete negative values, and V_{DS} was swept across a range. The corresponding I_D was measured.

The circuit configuration is illustrated in Figure 29.

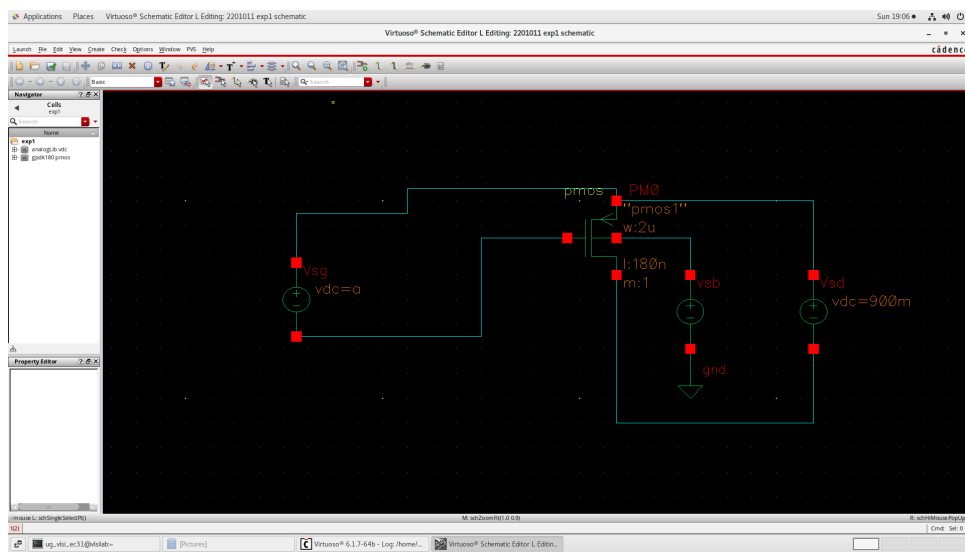


Figure 6: Circuit Diagram for PMOS Characteristics Measurement

Results

The experimental data were plotted to visualize the PMOS transistor's behavior. The results are presented in the following figures: - Figure 7: Input characteristic curve showing I_D versus V_{GS} . - Figure 8: Parametric input characteristic, likely illustrating I_D versus V_{GS} under varying conditions (e.g., different V_{DS} values). - Figure 9: Output characteristic curves displaying I_D versus V_{DS} for multiple fixed V_{GS} values. - Figure 10: Parametric output characteristic, possibly showing additional parameter variations.

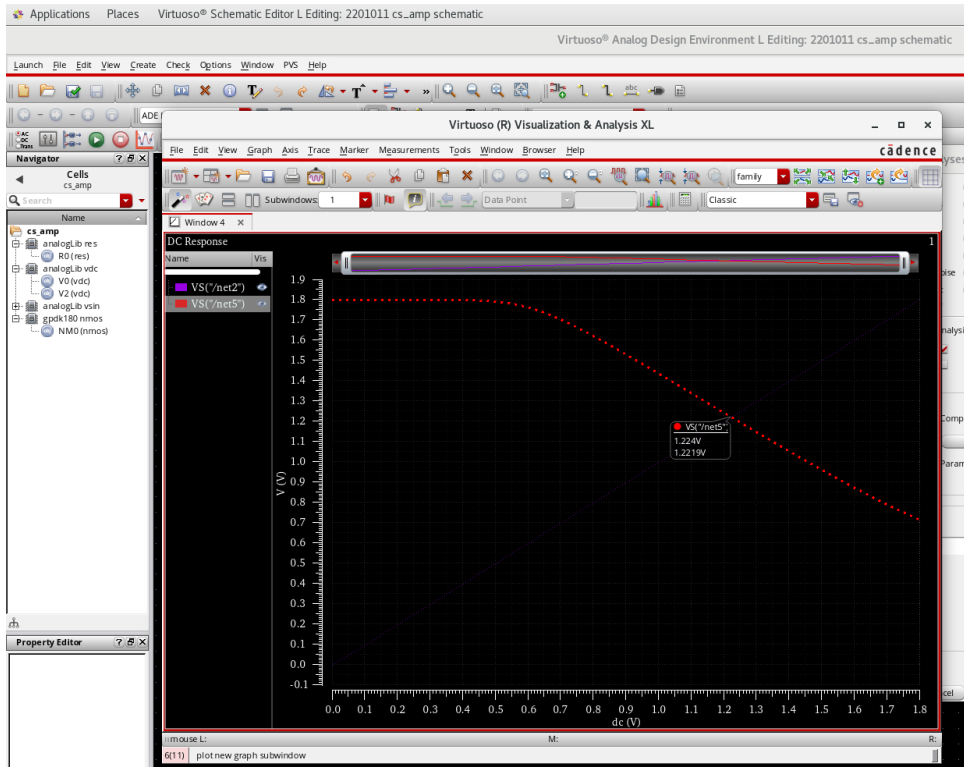


Figure 7: Input Characteristic: I_D vs. V_{GS} for PMOS Transistor

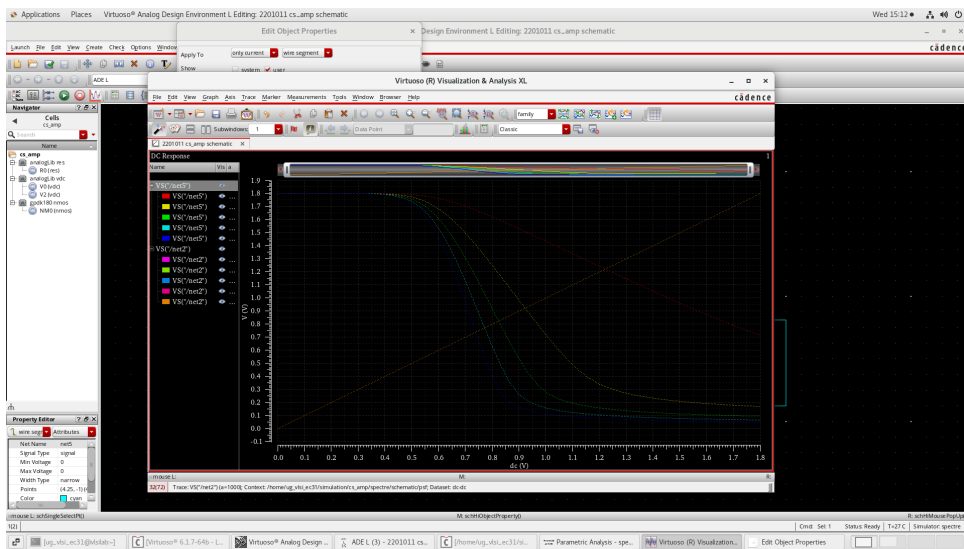


Figure 8: Parametric Input Characteristic: I_D vs. V_{GS} for PMOS Transistor

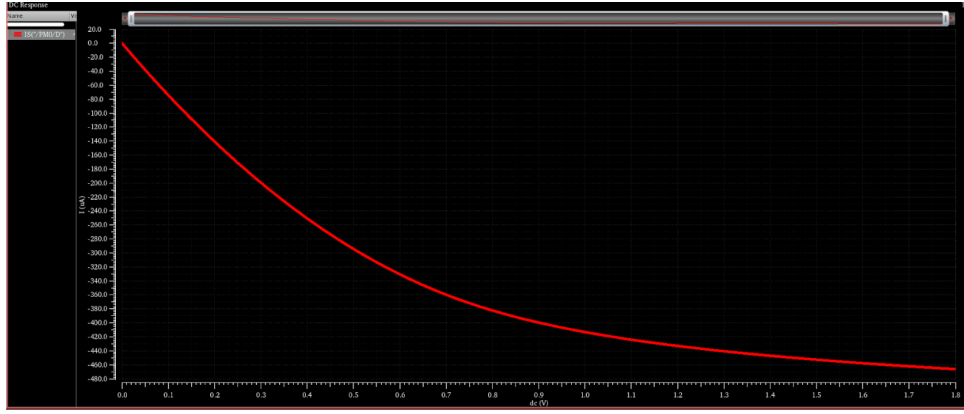


Figure 9: Output Characteristic: I_D vs. V_{DS} for PMOS Transistor

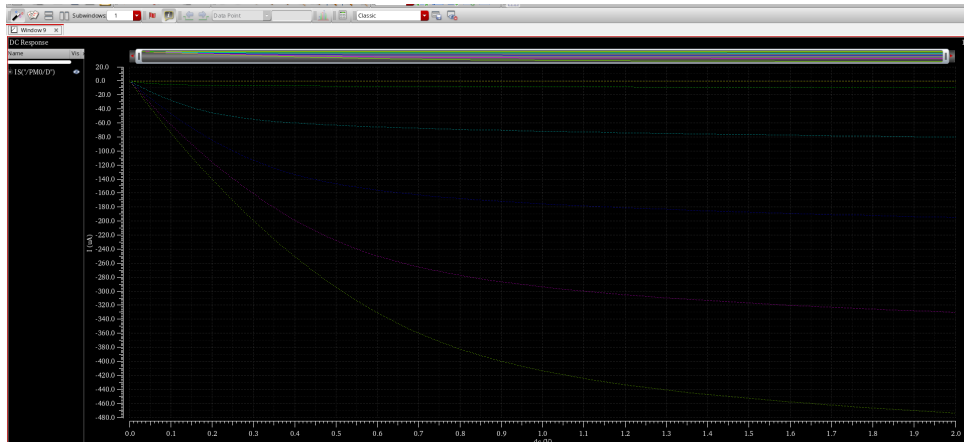


Figure 10: Parametric Output Characteristic: I_D vs. V_{DS} for PMOS Transistor

Discussion

The input characteristic curve (Figure 7) exhibits a quadratic increase in I_D with V_{GS} becoming sufficiently negative (below V_t), consistent with the theoretical saturation region behavior for a PMOS transistor. This confirms the transistor's operation as predicted by the MOSFET equation.

The output characteristic curves (Figure 9) illustrate a clear transition from the linear region, where I_D rises with V_{DS} , to the saturation region, where I_D stabilizes. This behavior aligns with the expected performance for different negative V_{GS} values, underlining the transistor's utility in amplification applications.

The parametric plots (Figures 8 and 10) provide deeper insights, potentially showing how additional variables (e.g., temperature or device parameters) affect the characteristics. These results reinforce the theoretical framework and validate the experimental methodology.

Conclusion

This experiment successfully verified the input and output characteristics of a PMOS transistor. The input characteristics demonstrated a quadratic rise in drain current (I_D)

with increasing negative gate-to-source voltage (V_{GS}) below the threshold voltage, confirming saturation region behavior. The output characteristics revealed distinct linear and saturation regions as drain-to-source voltage (V_{DS}) varied, consistent with theoretical expectations for fixed negative V_{GS} values. These findings validate the MOSFET's operational principles and affirm its applicability in amplification and switching circuits.

Experiment-3: Analysis of DC, AC, and Transient Response of a CS Amplifier

Introduction

The objective of this experiment is to analyze the DC, AC, and transient response of a resistive load inverter using a sinusoidal input signal (VSIN) and to determine the magnitude gain and phase shift from the AC analysis. A resistive load inverter, constructed with an NMOS transistor and a resistor connected to its drain, is a fundamental building block in digital and analog circuits. This experiment evaluates the inverter's behavior under different analysis conditions, providing insights into its voltage transfer characteristics (VTC), switching dynamics, and frequency response. The results validate the inverter's functionality as a logic gate and its performance in signal processing applications.

Theory

A resistive load inverter consists of an NMOS transistor with a resistor (R_D) connected between the drain and the supply voltage (V_{DD}). The input voltage (V_{in}) is applied to the gate, and the output voltage (V_{out}) is taken at the drain. The inverter operates by inverting the input signal: a high V_{in} turns the NMOS ON, pulling V_{out} low, while a low V_{in} turns the NMOS OFF, allowing V_{out} to be pulled high through R_D .

DC Analysis

DC analysis determines the Voltage Transfer Characteristics (VTC), which plot V_{out} versus V_{in} . The VTC reveals key parameters: - Switching Threshold (V_M): The point where $V_{in} = V_{out}$. - Logic Levels: High output voltage (V_{OH}) when the NMOS is OFF, and low output voltage (V_{OL}) when the NMOS is ON. - Noise Margins: Derived from the VTC to assess the inverter's robustness.

The NMOS operates in different regions (cut-off, linear, saturation) depending on V_{in} , shaping the VTC curve.

Transient Analysis

Transient analysis examines the inverter's time-domain response to a dynamic input, here a sinusoidal signal (VSIN). It reveals: - Switching Behavior: How V_{out} transitions in response to V_{in} . - Propagation Delay: The time taken for V_{out} to respond to changes in V_{in} . - Inversion: Confirmation that V_{out} is the logical inverse of V_{in} .

The sinusoidal input tests the inverter's ability to handle continuous signals, highlighting any distortions or delays.

AC Analysis

AC analysis evaluates the inverter's small-signal frequency response using a sinusoidal input. Key metrics include: - Magnitude Gain ($|V_{out}/V_{in}|$): The ratio of output to input signal amplitude, expressed in decibels (dB) as $20 \log_{10}(|V_{out}/V_{in}|)$. It indicates

amplification or attenuation. - Phase Shift ($\angle V_{out}/V_{in}$): The phase difference between V_{out} and V_{in} , measured in degrees, reflecting the time delay introduced by the inverter.

These parameters are plotted against frequency to characterize the inverter's bandwidth and phase behavior, critical for its use in amplifiers or high-speed logic circuits.

Methodology

The experimental setup involved a resistive load inverter circuit with an NMOS transistor, a load resistor (R_D), and a supply voltage (V_{DD}). The circuit was analyzed using simulation tools (e.g., SPICE) or a hardware setup with the following procedures: - DC Analysis: V_{in} was swept from 0 to V_{DD} , and V_{out} was measured to plot the VTC. - Transient Analysis: A sinusoidal input (VSIN) with specified amplitude, frequency, and DC offset was applied to the gate. V_{in} and V_{out} were recorded over time to observe the inverter's dynamic response. - AC Analysis: A small-signal sinusoidal input was applied, and V_{out} was measured across a range of frequencies. Magnitude gain and phase shift were calculated and plotted.

The circuit configuration is shown in Figure 29.

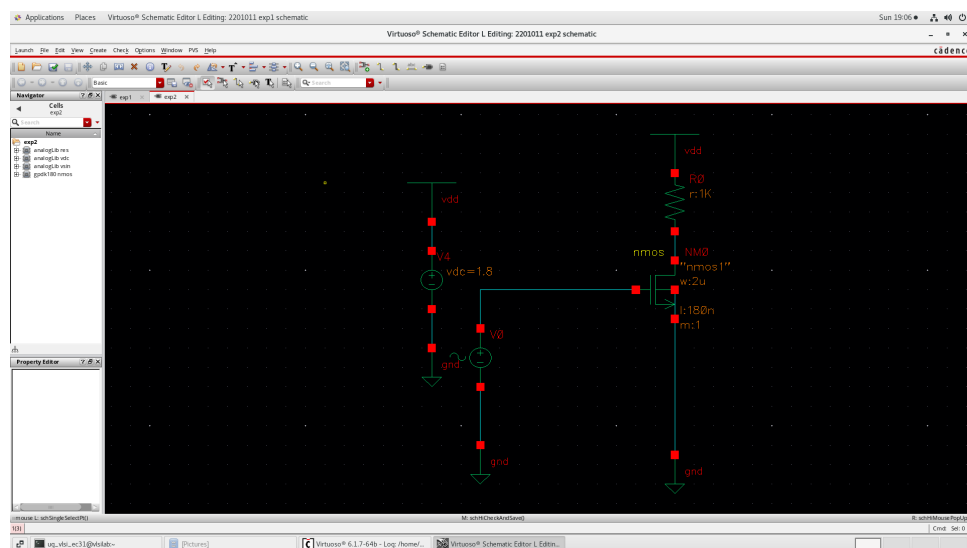


Figure 11: Circuit Diagram of Resistive Load CS Amplifier

Results

The experiment yielded the following results, visualized in the figures below: - Figure 16: Voltage Transfer Characteristics (VTC) curve, plotting V_{out} versus V_{in} . - Figure 17: Transient response, showing V_{in} (sinusoidal) and V_{out} waveforms over time. - Figure 14: AC analysis, combining plots of magnitude gain ($|V_{out}/V_{in}|$) in dB and phase shift ($\angle V_{out}/V_{in}$) in degrees versus frequency.

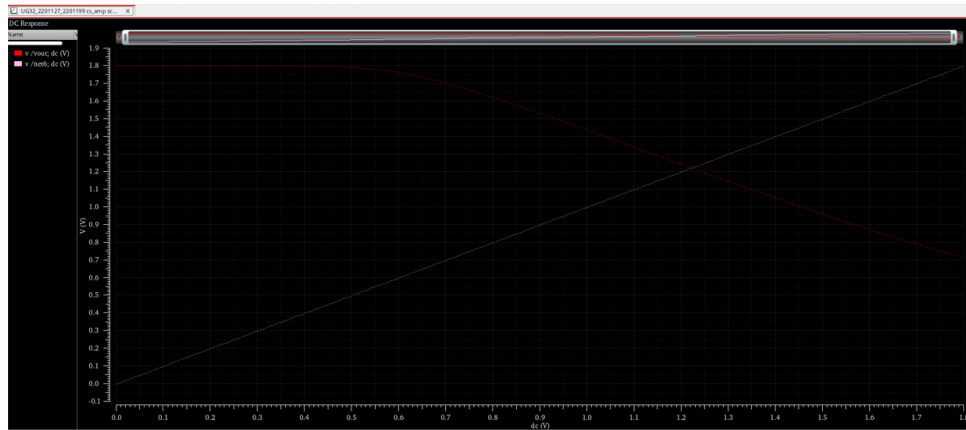


Figure 12: DC Analysis: Voltage Transfer Characteristics (VTC) of the Inverter

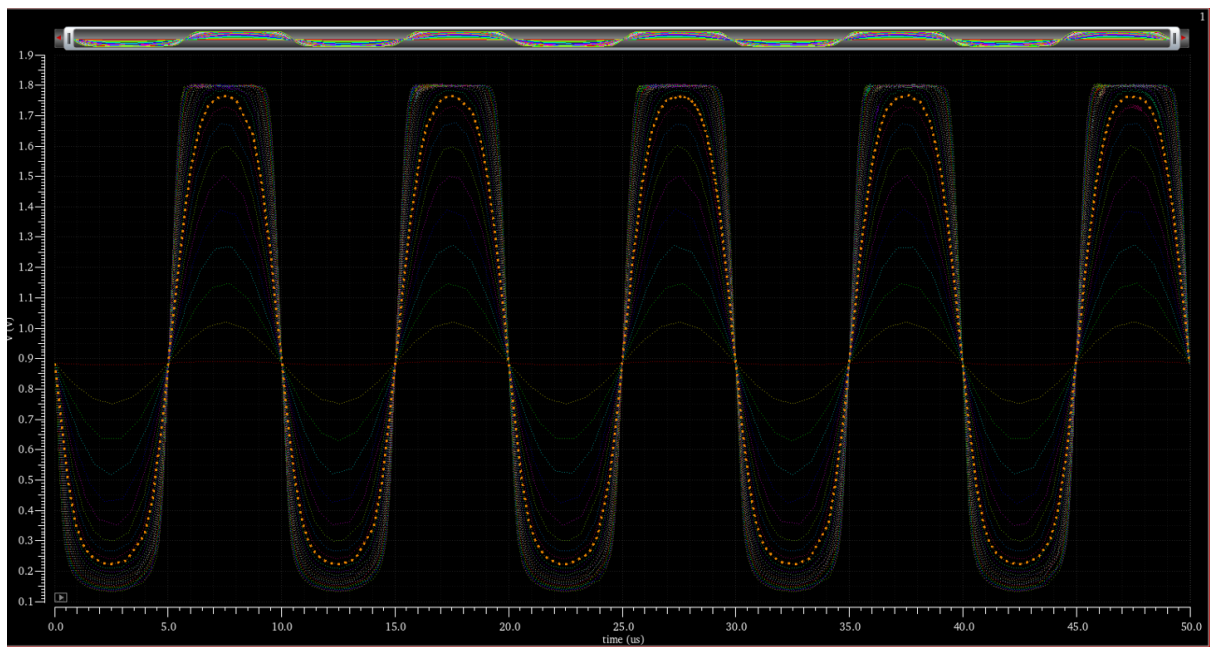


Figure 13: Transient Analysis: Input and Output Waveforms for Sinusoidal Input



Figure 14: AC Analysis: Magnitude Gain and Phase Shift vs. Frequency

Discussion

The VTC curve (Figure 16) exhibits the expected inverter behavior: a sharp transition from high to low V_{out} as V_{in} increases beyond the switching threshold. The curve confirms well-defined logic levels (V_{OH} and V_{OL}) and a clear switching point, indicating robust digital operation.

The transient response (Figure 17) demonstrates proper signal inversion, with V_{out} mirroring the inverse of the sinusoidal V_{in} . The waveform reveals the inverter's switching dynamics, including any propagation delay or distortion introduced by the resistive load and NMOS characteristics.

The AC analysis (Figure 14) provides critical insights into the inverter's frequency response. The magnitude gain plot shows whether the inverter amplifies or attenuates the input signal across frequencies, with potential roll-off at higher frequencies due to parasitic capacitances. The phase shift plot indicates increasing lag as frequency rises, consistent with the inverter's time-domain delays. These results are essential for evaluating the inverter's performance in high-frequency applications or as a small-signal amplifier.

Conclusion

This experiment successfully investigated the DC, AC, and transient characteristics of a resistive-load inverter, with emphasis on its behavior as a Common-Source (CS) amplifier. The DC analysis revealed a well-defined voltage transfer characteristic, confirming the presence of a distinct switching threshold and showcasing the inverter's ability to operate in both cutoff and saturation regions. Transient analysis demonstrated correct inversion and dynamic switching behavior in response to time-varying inputs, including observable propagation delays. AC analysis highlighted the amplifier's frequency response, revealing

key parameters such as gain and phase shift—critical for assessing its analog performance. Overall, the results align with theoretical expectations and reinforce the dual functionality of the resistive-load inverter in both digital logic and analog amplification contexts.

Experiment-4: Analysis of DC and Transient Response of a CMOS Inverter

Introduction

The objective of this experiment is to analyze the DC and transient response of a CMOS inverter and to determine its symmetric Voltage Transfer Characteristics (VTC), as well as the propagation delay times (TPHL and TPLH), using DC simulation and transient analysis. The CMOS (Complementary Metal-Oxide-Semiconductor) inverter, comprising an NMOS and a PMOS transistor, is a fundamental component in digital circuits due to its low power consumption and robust switching behavior. This experiment evaluates the inverter's static and dynamic performance, providing insights into its switching threshold, logic inversion, and timing characteristics, which are critical for digital logic applications.

Theory

A CMOS inverter consists of an NMOS transistor (pull-down) and a PMOS transistor (pull-up) connected in series between the supply voltage (V_{DD}) and ground. The input voltage (V_{in}) is applied to both transistor gates, and the output voltage (V_{out}) is taken at the common drain node. The inverter performs logic inversion: - When V_{in} is high, the NMOS turns ON and the PMOS turns OFF, pulling V_{out} low (close to 0). - When V_{in} is low, the PMOS turns ON and the NMOS turns OFF, pulling V_{out} high (close to V_{DD}).

DC Analysis

DC analysis determines the Voltage Transfer Characteristics (VTC), which plot V_{out} versus V_{in} . The VTC reveals: - Switching Threshold (V_M): The point where $V_{in} = V_{out}$, indicating the transition between logic states. - Symmetric Behavior: Due to complementary NMOS and PMOS operation, a well-designed CMOS inverter exhibits a symmetric VTC, with V_M ideally at $V_{DD}/2$. - Logic Levels: High output voltage (V_{OH}) and low output voltage (V_{OL}), defining the inverter's noise margins.

The symmetry of the VTC is influenced by the transistor sizing, specifically the width-to-length (W/L) ratios. In this experiment, the PMOS has a W/L ratio of 4, and the NMOS has a W/L ratio of 1, balancing the current-driving capabilities of both transistors.

Transient Analysis

Transient analysis examines the inverter's time-domain response to a dynamic input, here a sinusoidal signal (VSIN). It quantifies: - Switching Behavior: How V_{out} transitions in response to V_{in} , confirming logic inversion. - Propagation Delays: - TPHL: High-to-low propagation delay, the time taken for V_{out} to fall from high to the midpoint (e.g., 50% of V_{DD}) after V_{in} rises. - TPLH: Low-to-high propagation delay, the time taken for V_{out} to rise from low to the midpoint after V_{in} falls. - Symmetry in Delays: Balanced TPHL and TPLH values indicate symmetric switching, a hallmark of well-designed CMOS inverters.

The transient response depends on the transistor parameters and load capacitance, with the W/L ratios affecting the charging and discharging rates.

Methodology

The experimental setup involved a CMOS inverter circuit with an NMOS transistor ($W/L = 1$) and a PMOS transistor ($W/L = 4$), connected between V_{DD} and ground. The circuit was analyzed using simulation tools (e.g., SPICE) or a hardware setup with the following procedures:

- DC Parametric Analysis: V_{in} was swept from 0 to V_{DD} , and V_{out} was measured to plot the VTC, focusing on the symmetric transfer curve and switching threshold.
- DC VTC Analysis: Specific attention was given to the point where $V_{in} = V_{out} = 0.9$, verifying the balanced transition between NMOS and PMOS conduction states.
- Transient Analysis: A sinusoidal input (VSIN) with specified amplitude, frequency, and DC offset was applied to the gate. V_{in} and V_{out} were recorded over time to observe switching behavior and measure TPHL and TPLH.

The circuit configuration is shown in Figure 29.

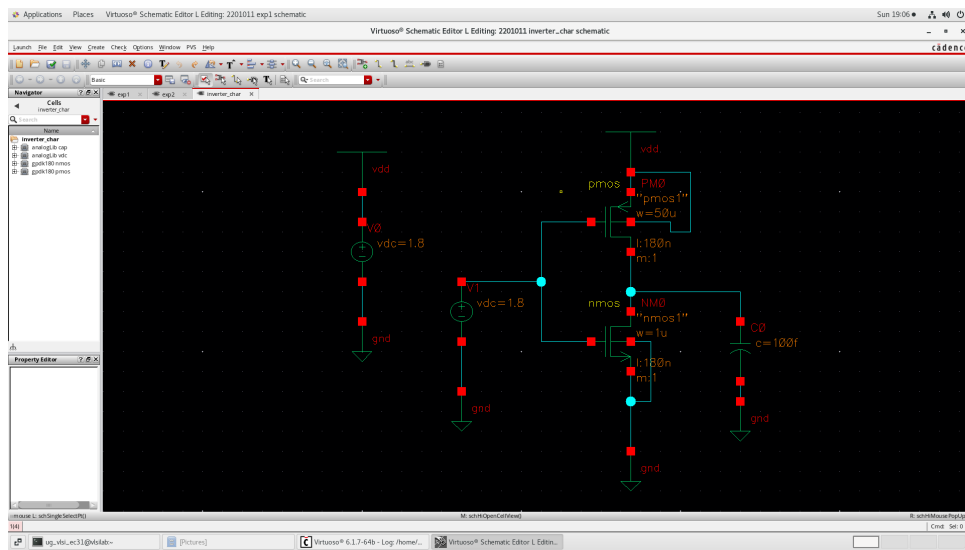


Figure 15: Circuit Diagram of CMOS Inverter

Results

The experiment produced the following results, visualized in the figures below:

- Figure ?? : DC parametric analysis, plotting V_{out} versus V_{in} .
- Figure 16: DC VTC analysis, showing the symmetric transfer curve with the switching threshold and the point at $V_{in} = V_{out} = 0.9$.
- Figure 17: Transient analysis, displaying V_{in} (sinusoidal) and V_{out} waveforms, with propagation delays $TPHL = 0.1503$ and $TPLH = 0.1530$.

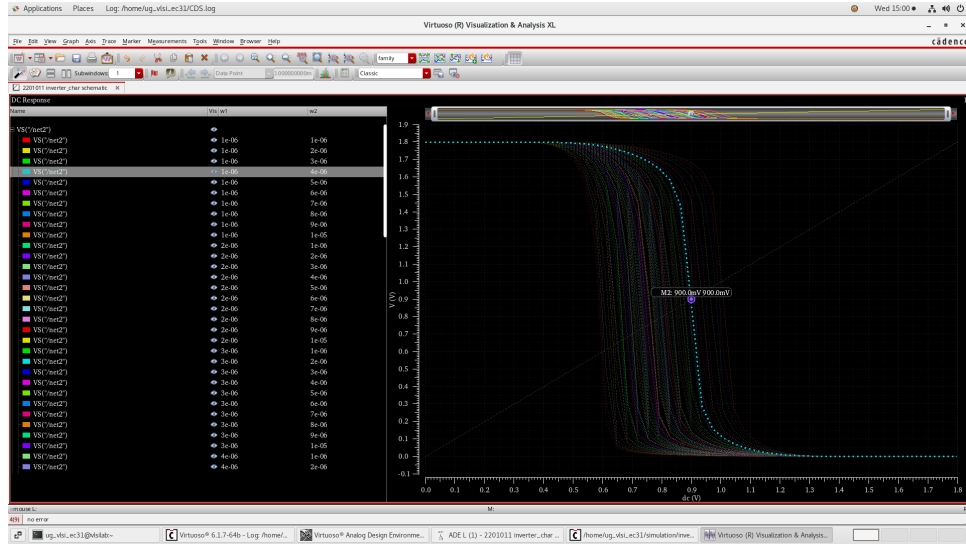


Figure 16: DC VTC Analysis: Symmetric Voltage Transfer Characteristics of the CMOS Inverter

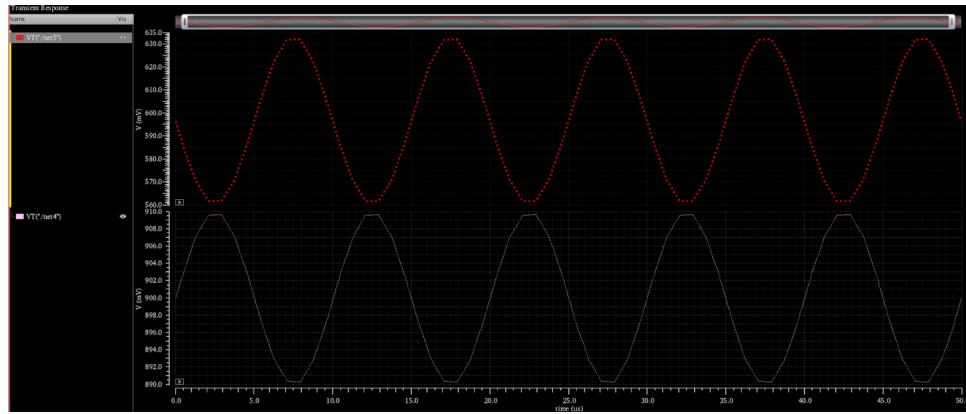


Figure 17: Transient Analysis: Input and Output Waveforms with Propagation Delays

Discussion

The DC parametric analysis (Figure ??) illustrates the inverter's response across the full range of V_{in} , laying the groundwork for the VTC. The VTC curve (Figure 16) exhibits a symmetric shape, with a switching threshold at $V_{in} = V_{out} = 0.9$. This point indicates a balanced transition, where the NMOS and PMOS transistors have equal current-driving capabilities, influenced by the W/L ratios (4 for PMOS, 1 for NMOS). The symmetry confirms optimal transistor sizing for equal pull-up and pull-down strengths.

The transient analysis (Figure 17) demonstrates clear logic inversion, with V_{out} transitioning oppositely to V_{in} . The measured propagation delays, $TPHL = 0.1503$ and $TPLH = 0.1530$, are nearly equal, reinforcing the inverter's symmetric switching behavior. The close values suggest that the PMOS and NMOS transistors are well-matched, minimizing timing disparities in high-to-low and low-to-high transitions.

These results align with theoretical expectations for a CMOS inverter, where complementary transistor operation ensures low power consumption and robust performance.

The W/L ratio configuration enhances current drive, contributing to the observed delay characteristics.

Conclusion

This experiment successfully analyzed the DC and transient response of a CMOS inverter. The DC parametric and VTC analyses confirmed a symmetric transfer curve with a well-defined switching threshold at $V_{in} = V_{out} = 0.9$, validated by the W/L ratios of 4 (PMOS) and 1 (NMOS). The transient analysis verified correct logic inversion and measured propagation delays of $TPHL = 0.1503$ and $TPLH = 0.1530$, indicating balanced switching performance. These findings demonstrate the CMOS inverter's effectiveness as a logic gate, with symmetric characteristics and appropriate timing for digital circuit applications.

Experiment-5: Analysis of DC Voltage Transfer Characteristics and Truth Table Verification of NAND and NOR Gates

Introduction

The objective of this experiment is to analyze the DC Voltage Transfer Characteristics (VTC) of NAND and NOR gates and verify their truth tables using a VPULSE input source. NAND and NOR gates, implemented using CMOS technology with PMOS and NMOS transistors, are universal logic gates fundamental to digital circuit design. This experiment evaluates the static switching behavior through VTC plots and confirms dynamic logic functionality by verifying the truth tables, ensuring the gates operate as expected for all input combinations.

Theory

NAND and NOR gates are constructed using complementary PMOS and NMOS transistors, leveraging their configurations to achieve the desired logic functions.

NAND Gate

- Configuration: - NMOS Transistors: Connected in parallel at the input stage, pulling the output low when all inputs are high. - PMOS Transistors: Connected in series at the output stage, pulling the output high unless all inputs are high. - Truth Table: Outputs low (0) only when all inputs are high (1); otherwise, outputs high (1). - VTC: The VTC plots output voltage (V_{out}) versus input voltage (V_{in}), showing inverter-like switching behavior for specific input combinations.

NOR Gate

- Configuration: - NMOS Transistors: Connected in series at the input stage, pulling the output low when any input is high. - PMOS Transistors: Connected in parallel at the output stage, pulling the output high only when all inputs are low. - Truth Table: Outputs high (1) only when all inputs are low (0); otherwise, outputs low (0). - VTC: The VTC illustrates output switching as a function of input voltage, reflecting the gate's logic behavior.

DC and Transient Analysis

- DC Analysis: Determines the VTC by sweeping one input voltage while fixing others, revealing the gate's switching threshold and logic levels. - Transient Analysis: Uses VPULSE signals (pulse waveforms) to simulate input combinations, verifying the truth table by observing V_{out} over time.

Methodology

The experimental setup involved CMOS-based NAND and NOR gate circuits, each with two inputs (A and B). The analysis was performed using simulation tools (e.g., SPICE) or hardware with the following procedures:

- DC VTC Analysis: - For the NAND gate, one input (V_A or V_B) was swept from 0 to V_{DD} , with the other input fixed at logic high or low, and V_{out} was measured.
- For the NOR gate, a similar sweep was performed, adjusting input conditions to capture the switching behavior.
- Truth Table Verification: - VPULSE signals were applied to inputs A and B, generating all possible input combinations (00, 01, 10, 11).
- The output voltage (V_{out}) was recorded over time to confirm the truth table for both gates.

The circuit configurations are shown in Figure 29.

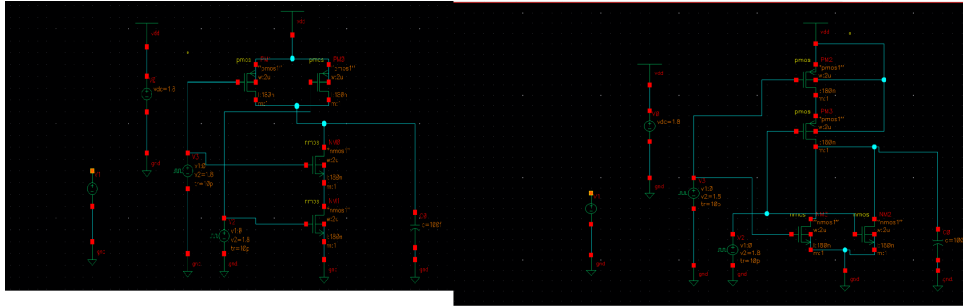


Figure 18: Circuit Diagram of NAND and NOR Gates

Results

The experiment yielded the following results, visualized in the figures below:

- Figure 19: DC VTC of the NAND gate, plotting V_{out} versus V_{in} .
- Figure 20: DC VTC of the NOR gate, plotting V_{out} versus V_{in} .
- Figure 21: Truth table verification for the NAND gate, showing output waveforms for VPULSE inputs.
- Figure 22: Truth table verification for the NOR gate, showing output waveforms for VPULSE inputs.

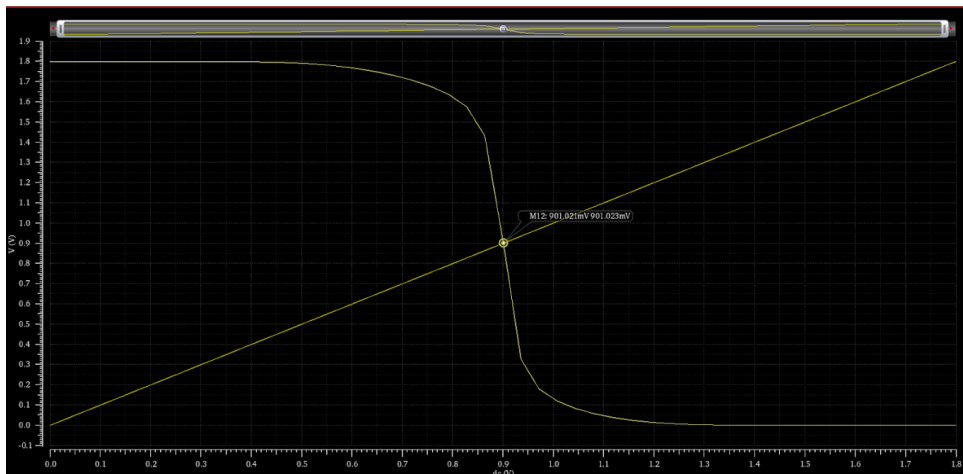


Figure 19: DC VTC of NAND Gate: Voltage Transfer Characteristics

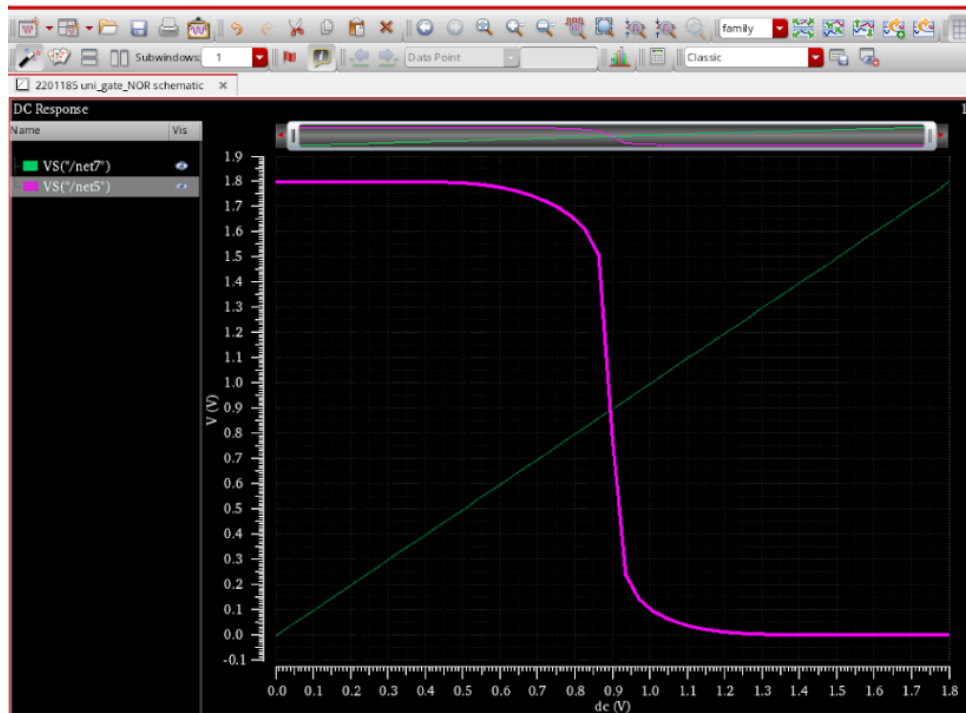


Figure 20: DC VTC of NOR Gate: Voltage Transfer Characteristics

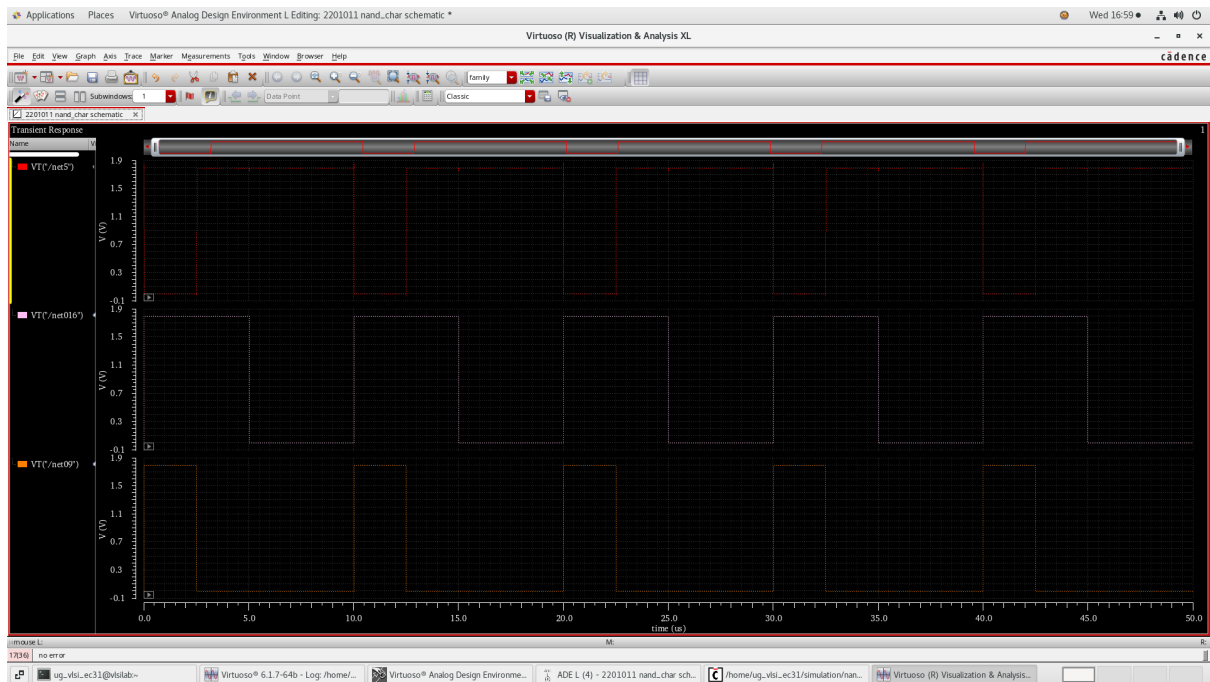


Figure 21: Truth Table Verification for NAND Gate: Output Waveforms

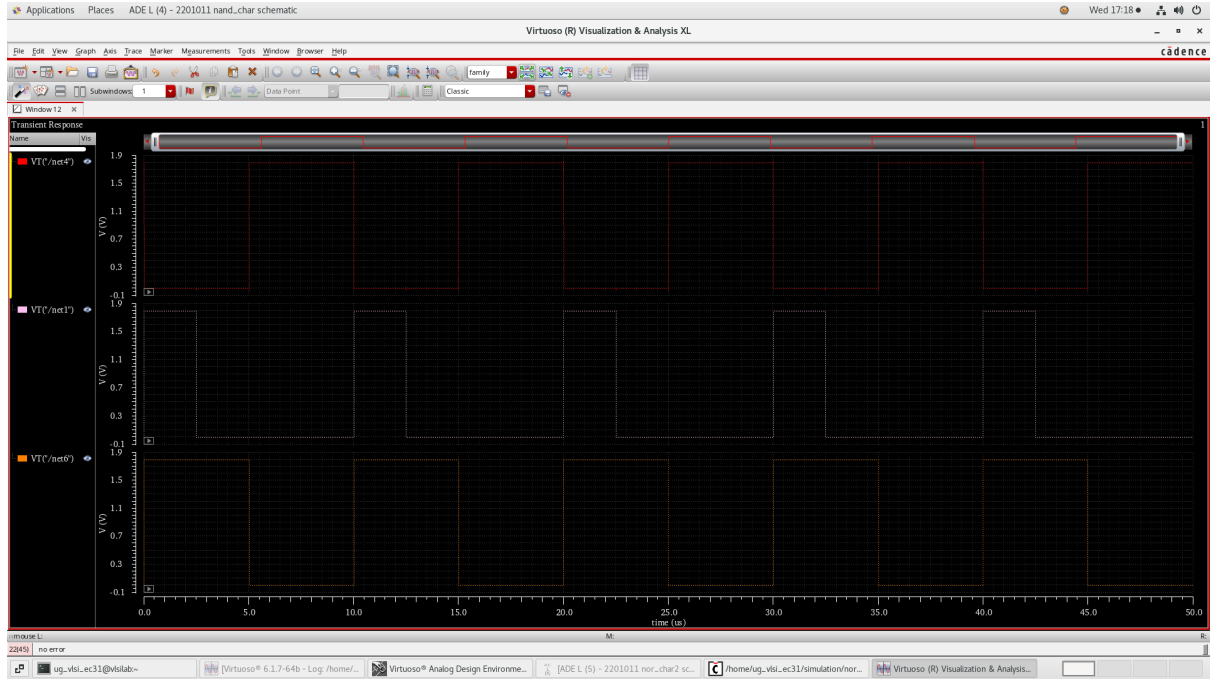


Figure 22: Truth Table Verification for NOR Gate: Output Waveforms

Discussion

The VTC plot for the NAND gate (Figure 19) shows a sharp transition from high to low V_{out} when both inputs are high, consistent with the parallel NMOS and series PMOS configuration. The switching threshold is well-defined, indicating robust logic operation.

The VTC plot for the NOR gate (Figure 20) demonstrates a transition from high to low V_{out} when any input is high, aligning with the series NMOS and parallel PMOS arrangement. The curve confirms the gate's sensitivity to input changes.

The truth table verification (Figures 21 and 22) confirms correct logic behavior. For the NAND gate, V_{out} is low only when both inputs are high (11); for the NOR gate, V_{out} is high only when both inputs are low (00). The VPULSE waveforms accurately reflect all input combinations, validating the gates' functionality.

These results align with theoretical expectations, demonstrating the effectiveness of CMOS implementations for universal logic gates.

Conclusion

This experiment successfully analyzed the DC VTC and verified the truth tables of NAND and NOR gates. The VTC plots for both gates exhibited expected switching behavior with clear thresholds, confirming their static performance. The truth table verification using VPULSE inputs validated the dynamic logic functionality, with outputs matching the expected values for all input combinations. These findings underscore the reliability of CMOS-based NAND and NOR gates in digital circuit design.

Experiment-6: Symbol Formation and Truth Table Verification for NAND, NOR, D Flip-Flop, and NOT Gates

Introduction

The aim of this experiment is to form symbols for NAND, NOR, D flip-flop, and NOT gates and verify their truth tables using appropriate input signals. Logic gates and flip-flops are the building blocks of digital circuits, each with standardized schematic symbols representing their functionality. This experiment focuses on creating accurate symbols and confirming their logical behavior through truth table verification, essential for understanding and designing digital systems.

Theory

Each logic element has a distinct symbol and truth table defining its operation:

NAND Gate

- Symbol: An AND gate with an inversion bubble at the output. - Function: Outputs low (0) only when all inputs are high (1); otherwise, outputs high (1). - Truth Table: For two inputs (A, B), output = $\overline{A \cdot B}$.

NOR Gate

- Symbol: An OR gate with an inversion bubble at the output. - Function: Outputs high (1) only when all inputs are low (0); otherwise, outputs low (0). - Truth Table: For two inputs (A, B), output = $\overline{A + B}$.

D Flip-Flop

- Symbol: A rectangle with D (data) and CLK (clock) inputs, and Q and $\overline{Q}$ outputs. - Function: Transfers the D input to Q on the rising edge of CLK, storing a single bit. - Truth Table: Q takes D's value at the clock edge; $\overline{Q}$ is the complement.

NOT Gate


- Symbol: A triangle with an inversion bubble at the output. - Function: Inverts the input (high to low, low to high). - Truth Table: For input A, output = $\overline{A}$.

Methodology


The experiment involved creating schematic symbols for each logic element using a circuit design tool and verifying their functionality: - Symbol Formation: Symbols for NAND,

NOR, D flip-flop, and NOT gates were drawn, adhering to standard conventions (e.g., inversion bubbles, input/output labels). - Truth Table Verification: - For NAND and NOR gates, two inputs (A, B) were driven with pulse signals to cover all combinations (00, 01, 10, 11). - For the D flip-flop, D and CLK inputs were applied, with CLK as a periodic pulse and D varying to test state transitions. - For the NOT gate, a single input was toggled between high and low. - Output waveforms were recorded to confirm the truth tables.

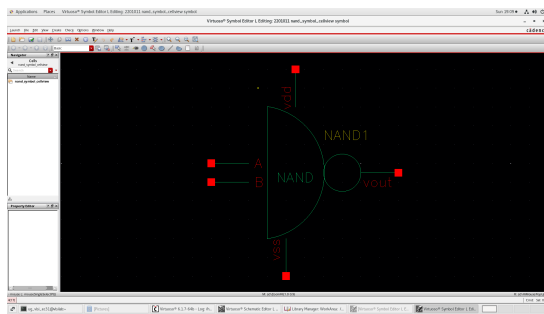
The symbol configurations are shown in Figure 23.




(a) NAND Gate Symbol

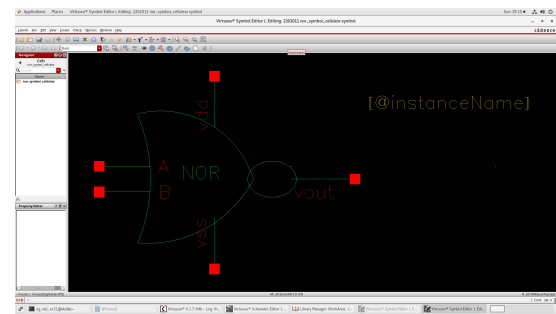

(b) NOR Gate Symbol

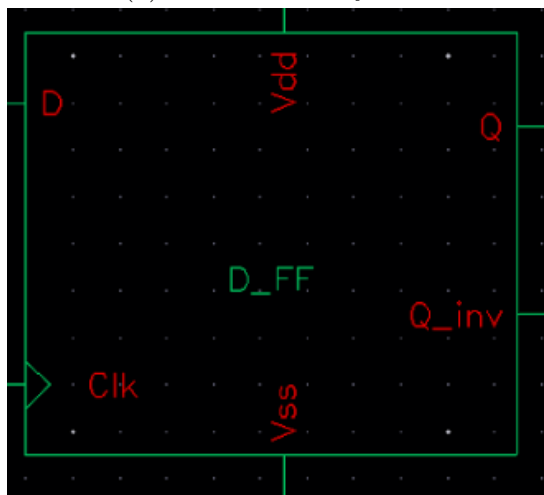

(c) D Flip-Flop Symbol

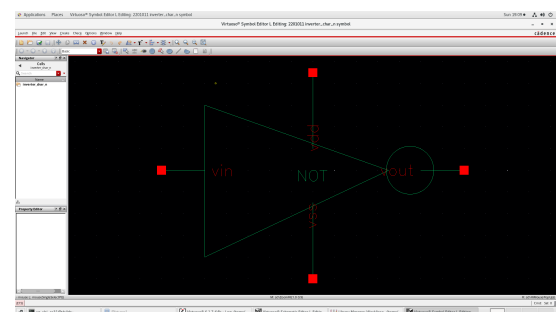

(d) NOT Gate Symbol

Figure 23: Circuit Diagram: Symbols for NAND, NOR, D Flip-Flop, and NOT Gates

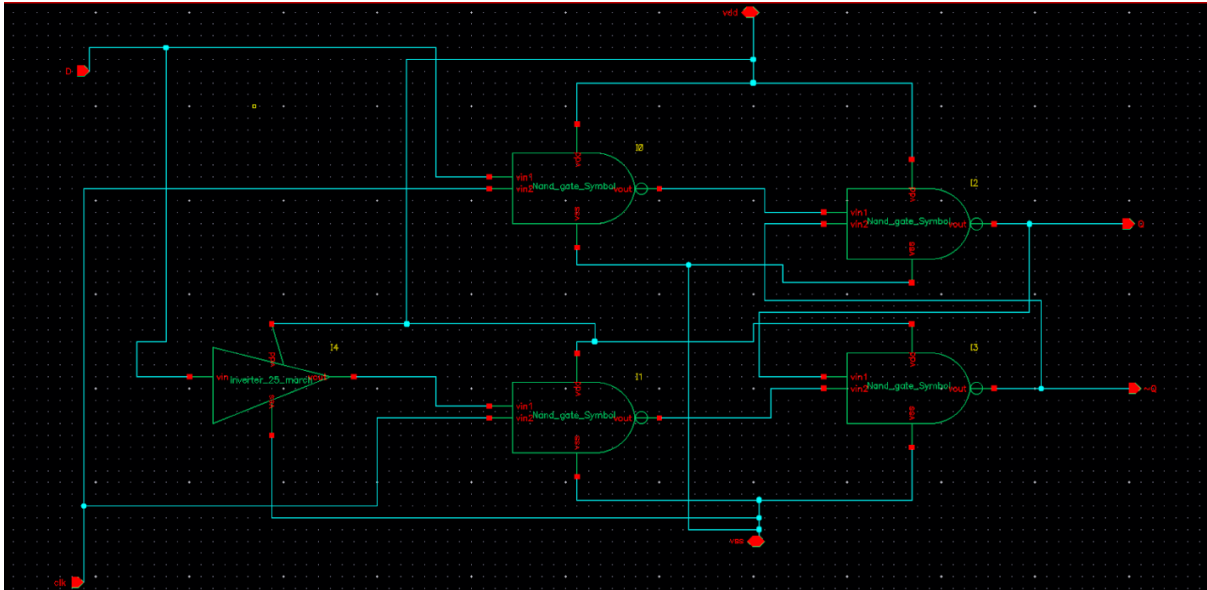


Figure 24: D Flip-Flop Design using Universal Designs

Results

The experiment produced the following results: - Figure 23: Diagram showing the created symbols for NAND, NOR, D flip-flop, and NOT gates. - Figure 28: Waveforms verifying the truth tables for all gates, capturing input and output signals.

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

(a) NAND Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

(b) NOR Gate

D	Q (Next)
0	0
1	1

(c) D Flip-Flop (Edge Triggered)

A	Y
0	1
1	0

(d) NOT Gate

Figure 25: Truth Tables for NAND, NOR, D Flip-Flop, and NOT Gates

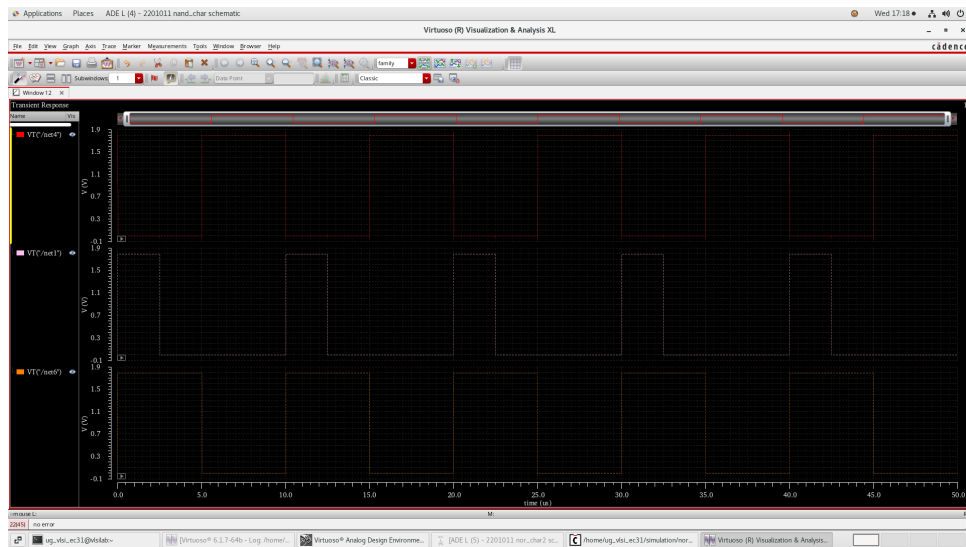


Figure 26: Truth Table Verification: Output Waveforms for NOR Gate



Figure 27: Truth Table Verification: Output Waveforms for NAND Gate

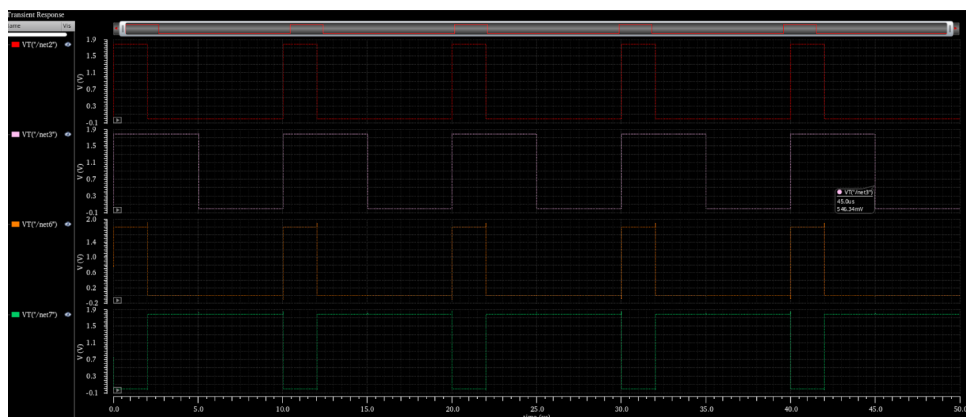


Figure 28: Truth Table Verification: Output Waveforms for D FF

Discussion

The symbols (above Figure) accurately represent the NAND, NOR, D flip-flop, and NOT gates, following standard conventions. The NAND and NOR symbols include inversion bubbles, the D flip-flop symbol clearly labels D, CLK, Q, and $\bar{Q}$, and the NOT gate symbol is a simple inverter.

The truth table verification (Figure 28) confirms correct operation: - NAND Gate: Low output only when $A = B = 1$. - NOR Gate: High output only when $A = B = 0$. - D Flip-Flop: Q follows D at CLK rising edges, with $\bar{Q}$ as the complement. - NOT Gate: Output is the inverse of the input.

These results validate the symbols' functionality, ensuring they can be used reliably in circuit schematics.

Conclusion

This experiment successfully formed symbols for NAND, NOR, D flip-flop, and NOT gates and verified their truth tables. The symbols adhered to standard representations, and the output waveforms confirmed expected logic behavior for all input combinations. These outcomes demonstrate proficiency in creating and validating logic elements, a critical skill in digital circuit design.

Experiment-7: Implementation and Analysis of a Current Mirror Circuit

Introduction

The aim of this experiment is to implement and analyze a PMOS current mirror circuit and understand the use of annotations in circuit simulation. A current mirror is a key analog circuit that replicates a reference current across multiple branches, widely used in biasing and amplification. This experiment verifies the mirroring functionality, ensures all transistors operate in saturation, and leverages annotations to confirm circuit performance, providing insights into analog design principles.

Theory

A current mirror copies the current from a reference transistor to one or more output transistors, maintaining a constant current proportional to the reference. In a PMOS current mirror:

- Reference Transistor: Sets the reference current (I_{REF}) based on its gate-source voltage (V_{GS}) and bias conditions.
- Output Transistors: Mirror I_{REF} by sharing the same V_{GS} and having matched width-to-length (W/L) ratios.
- Saturation Region: For accurate mirroring, all transistors must operate in saturation, where the drain current is:

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

- Annotations: Simulation tools provide annotations to display operating conditions (e.g., current, voltage, region), enabling verification of saturation and current matching.

The mirroring accuracy depends on transistor matching and proper biasing, ensuring identical V_{GS} across all transistors.

Methodology

The experimental setup involved a PMOS current mirror circuit with three PMOS transistors (PMOS1, PMOS2, PMOS3), where PMOS2 served as the reference transistor. The circuit was simulated or implemented with the following steps:

- Circuit Design: PMOS2 was biased to set I_{REF} , with its gate connected to the gates of PMOS1 and PMOS3 to mirror the current. All transistors had identical W/L ratios.
- Operating Condition Check: Annotations were used to verify that all transistors operated in saturation and to measure currents.
- Current Measurement: The currents through PMOS1 and PMOS3 were compared to I_{REF} (PMOS2) to confirm mirroring.

The circuit configuration is shown in Figure 29.

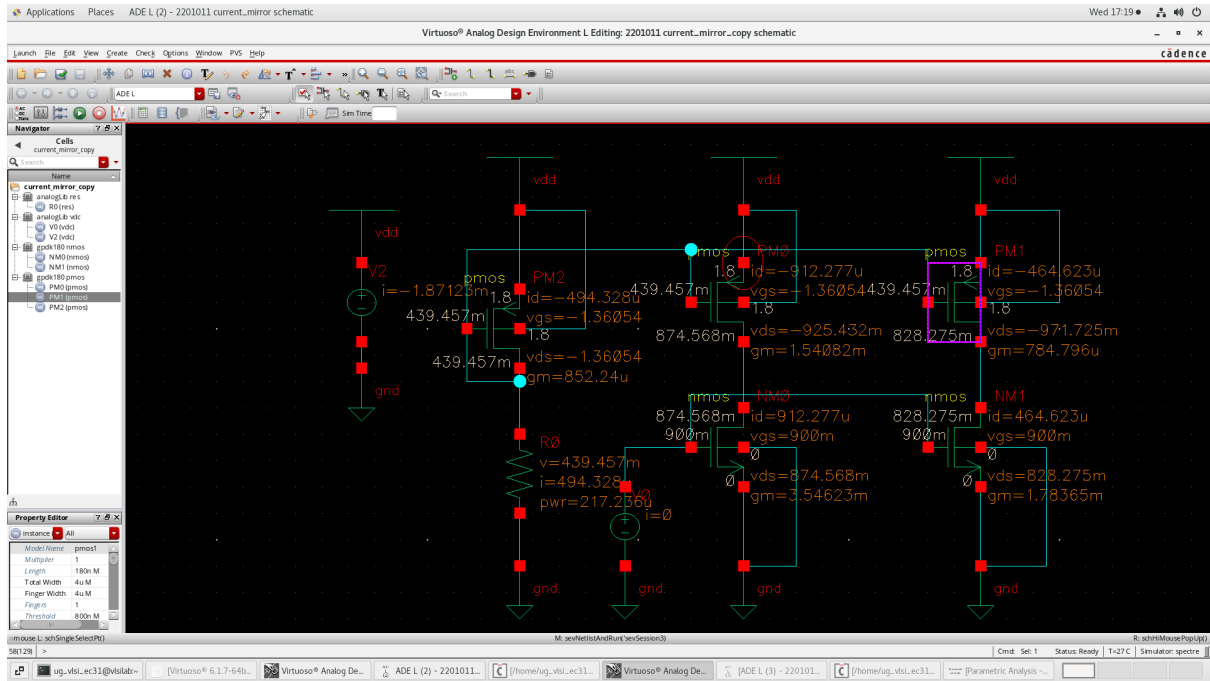


Figure 29: Circuit Diagram of PMOS Current Mirror

Results

The experiment produced the following results: - Figure 30: Diagram of the current mirror circuit, with annotations confirming saturation and current values. PMOS2 sets I_{REF} , mirrored to PMOS1 and PMOS3.

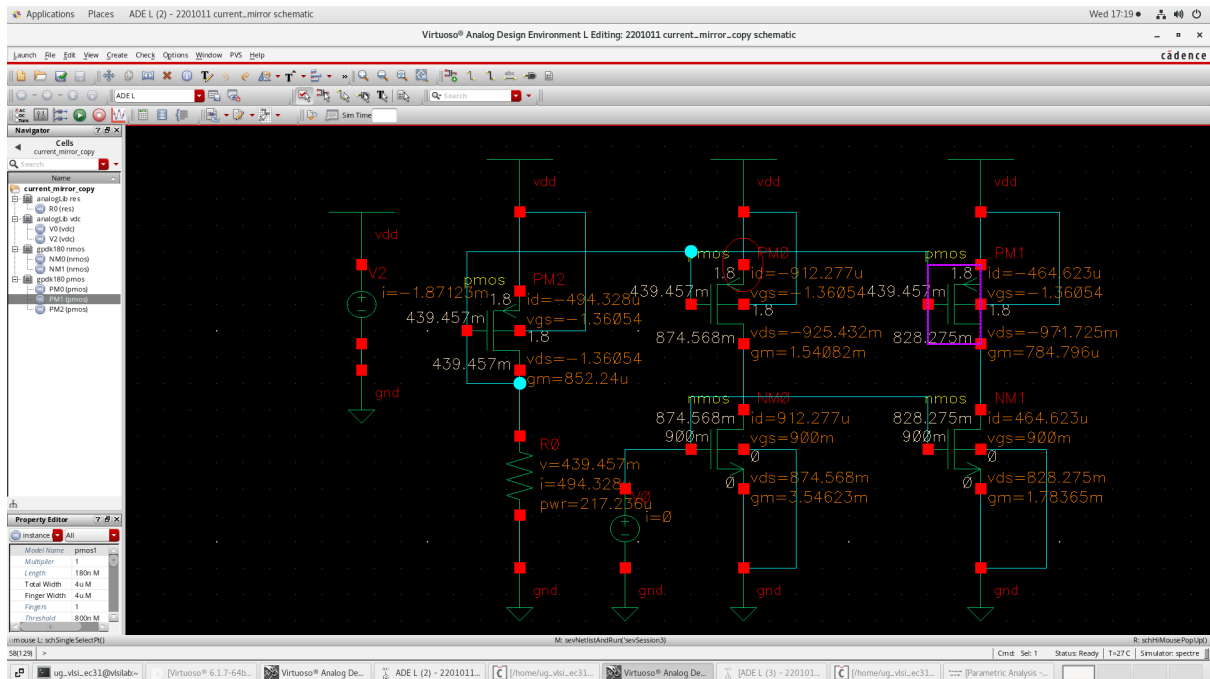


Figure 30: Current Mirror Circuit: Annotations Showing Saturation and Mirrored Currents

Discussion

The results (Figure 30) confirm that all PMOS transistors operated in saturation, as indicated by the annotations. PMOS2 established the reference current, which was accurately mirrored to PMOS1 and PMOS3, with currents closely matching due to identical W/L ratios and shared V_{GS} . The annotations provided critical insights into voltages, currents, and operating regions, simplifying the verification process.

The successful mirroring validates the circuit's design and the importance of transistor matching. Any minor discrepancies in current values could arise from simulation non-idealities or parasitic effects, but the results align with theoretical expectations for a PMOS current mirror.

Conclusion

This experiment successfully implemented and analyzed a PMOS current mirror circuit. Annotations confirmed that all transistors operated in saturation, and the reference current set by PMOS2 was accurately mirrored to PMOS1 and PMOS3. The use of annotations enhanced the analysis by providing clear operating condition data. These findings demonstrate the effectiveness of current mirrors in analog design and the utility of simulation tools in verifying circuit performance.